

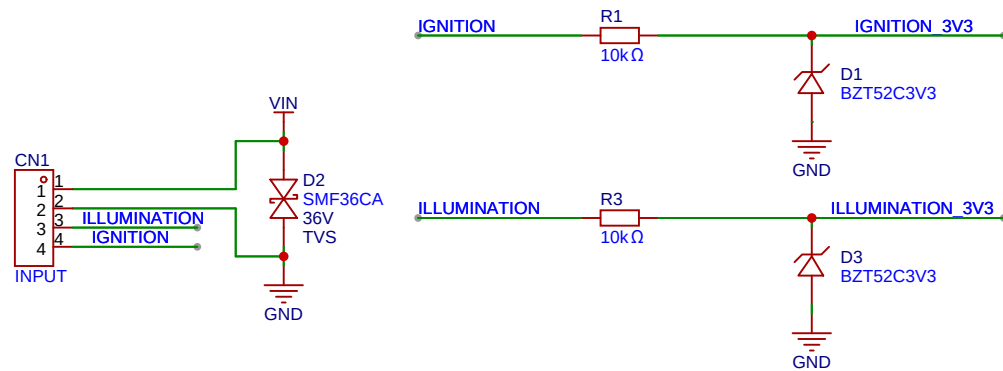


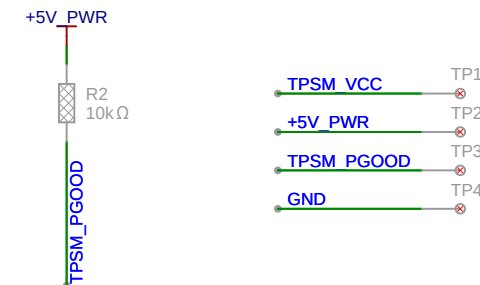


12V - 36V Input With Protection

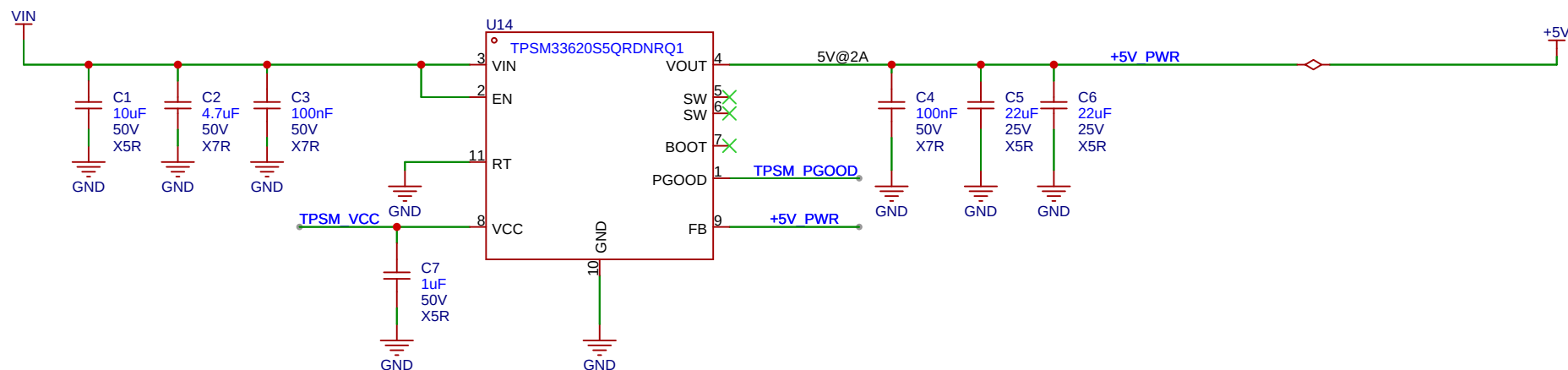

Pull-ups & Test Points





High Input Voltage Buck Converter

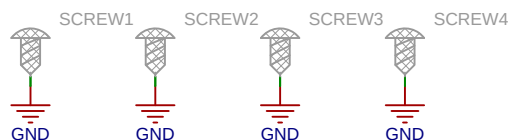

Mounting holes

Schematic	Schematic		Create at	2026-01-12
Board	ESP32P4C6DevBoard		Update at	2026-02-01
Drawn			Page	Main Power Converter
Reviewed			ESP32P4C6 Dev Board	
		Version	Size	Page 1 Total 9
		V1.0	A4	EasyEDA.com

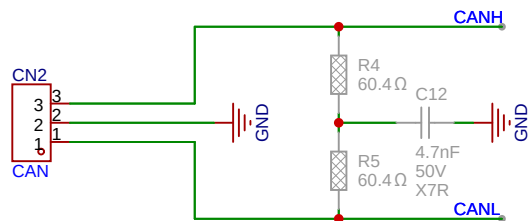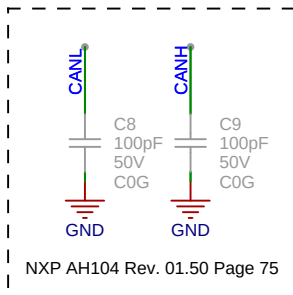


Populate termination if this node is at the CAN bus end; otherwise leave DNP.

CAN Termination




Test Points

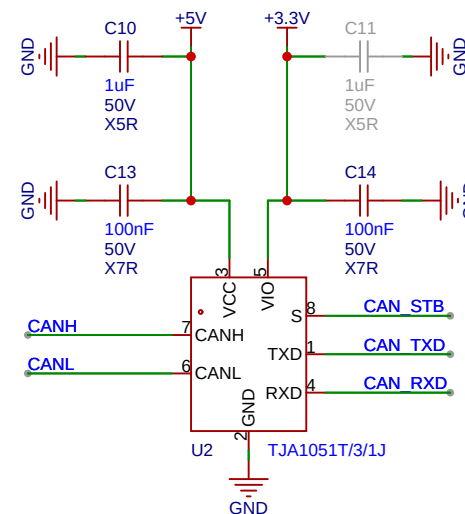


To MCU
CAN_STB
CAN_TXD
CAN_RXD

CAN Transceiver


Schematic	Schematic			Create at	2026-01-12
Board	ESP32P4C6DevBoard			Update at	2026-02-01
Drawn		ESP32P4C6 Dev Board			
Reviewed					
		Version	Size	Page 2 Total 9	
EasyEDA		V1.0	A4	EasyEDA.com	

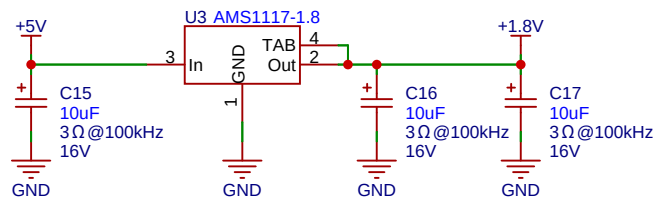

1.8V LDO

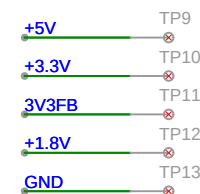


Test Points

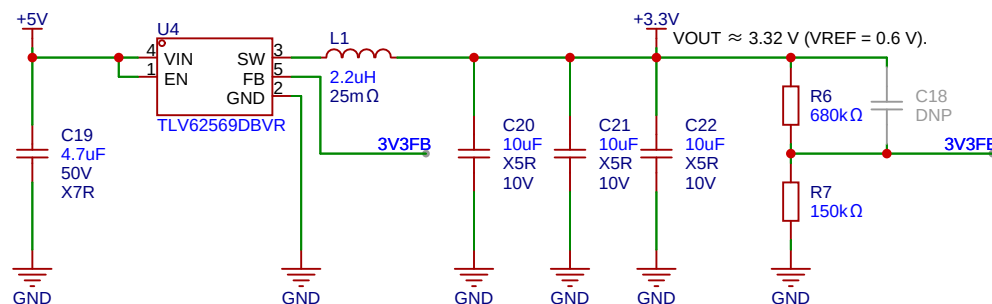


3.3V Rail Buck Converter

Schematic	Schematic			Create at	2026-01-12
Board	ESP32P4C6DevBoard			Update at	2026-02-01
Drawn	ESP32P4C6 Dev Board			Page	Power Rails
Reviewed					
		Version	Size	Page 3 Total 9	
		V1.0	A4	EasyEDA.com	

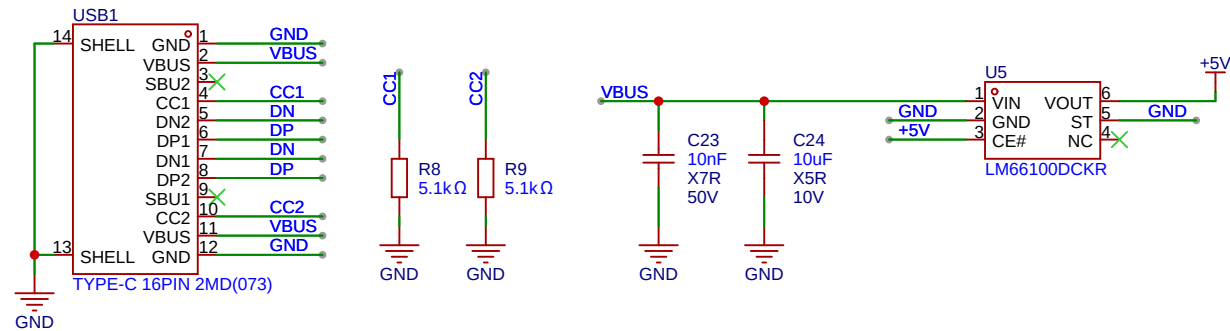


USB Input

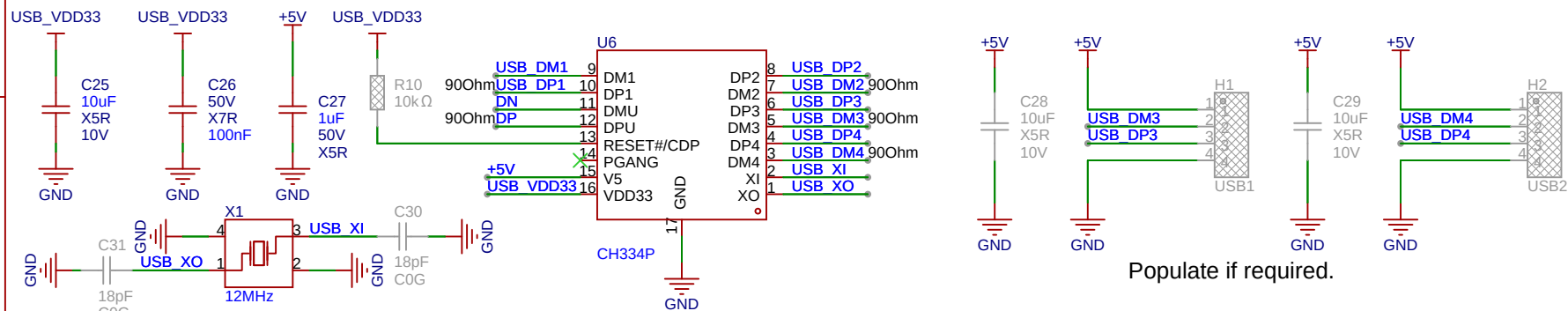

Capacitors are not required as per online examples

CH334P USB HUB


Test Points

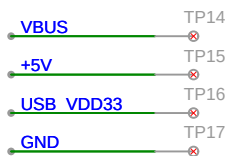


To MCU

USB_DM1
USB_DP1

Schematic	Schematic		Create at	2026-01-13
Board	ESP32P4C6DevBoard		Update at	2026-02-01
Drawn		ESP32P4C6 Dev Board		
Reviewed				
		Version	Size	Page 4 Total 9
		V1.0	A4	EasyEDA.com

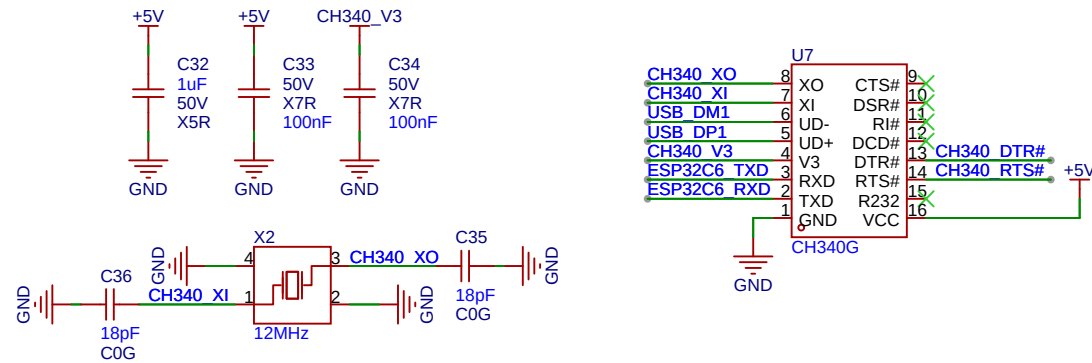

CH340G USB<->UART

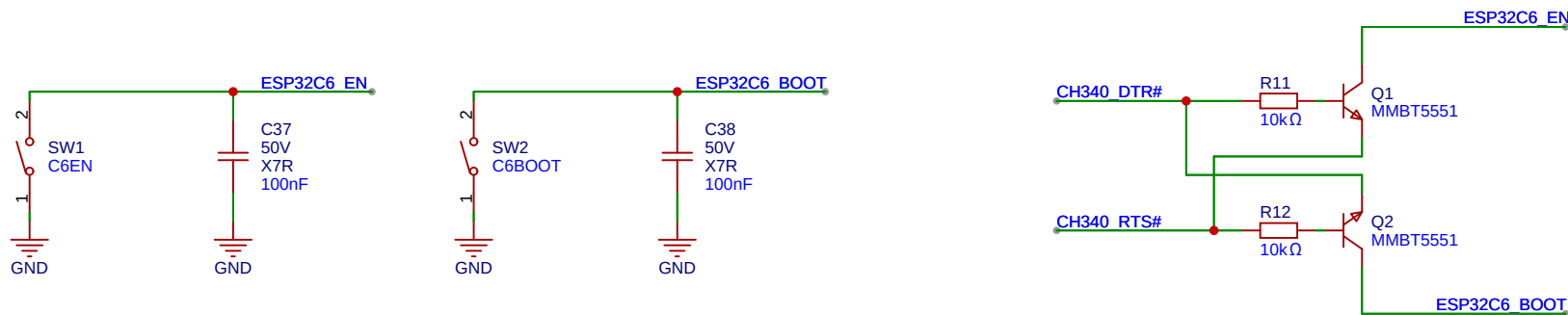



ESP32-C6 Downlaod Circuit

Test Points


ESP32C6_EN TP18
ESP32C6_BOOT TP19
ESP32C6_TXD TP20
ESP32C6_RXD TP21
GND TP22

To MCU
ESP32C6_EN
ESP32C6_BOOT
ESP32C6_TXD
ESP32C6_RXD



Schematic	Schematic		Create at	2026-01-14
Board	ESP32P4C6DevBoard		Update at	2026-02-01
Drawn			Page	ESP32-C6 USB-UART
Reviewed			ESP32P4C6 Dev Board	
		Version	Size	Page 5 Total 9
		V1.0	A4	EasyEDA.com

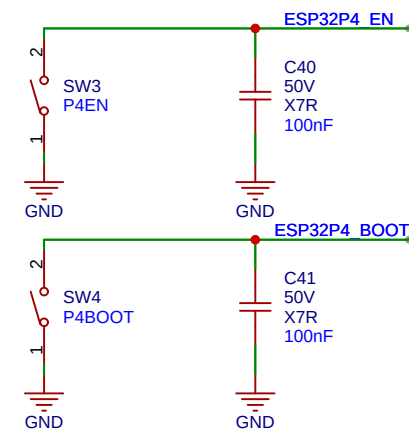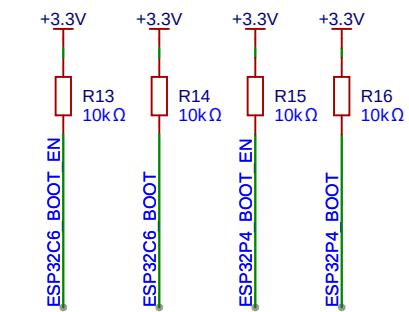


Strapping & Boot

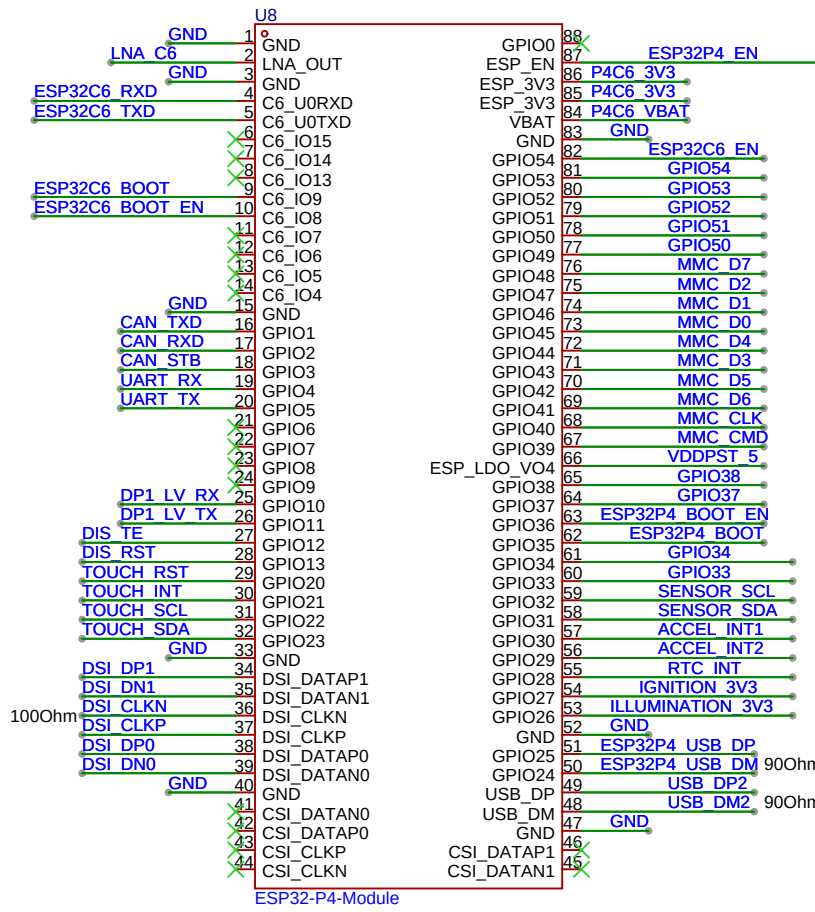

ESP32-P4-Module (Waveshare)

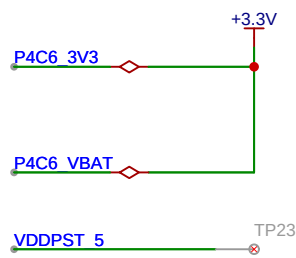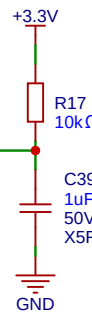


Power

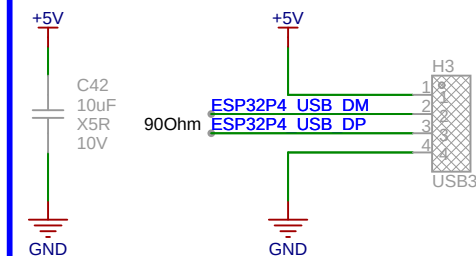





Populate if required.

ESP32-P4 USB Host

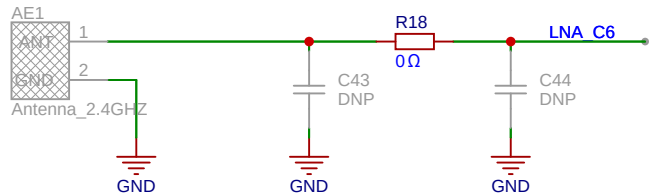


2.4GHz PCB Antenna



Schematic	Schematic			Create at	2026-01-14
Board	ESP32P4C6DevBoard			Update at	2026-02-01
Drawn	ESP32P4C6 Dev Board			Page	ESP32P4C6
Reviewed					
		Version	Size	Page 6 Total 9	
		V1.0	A4	EasyEDA.com	

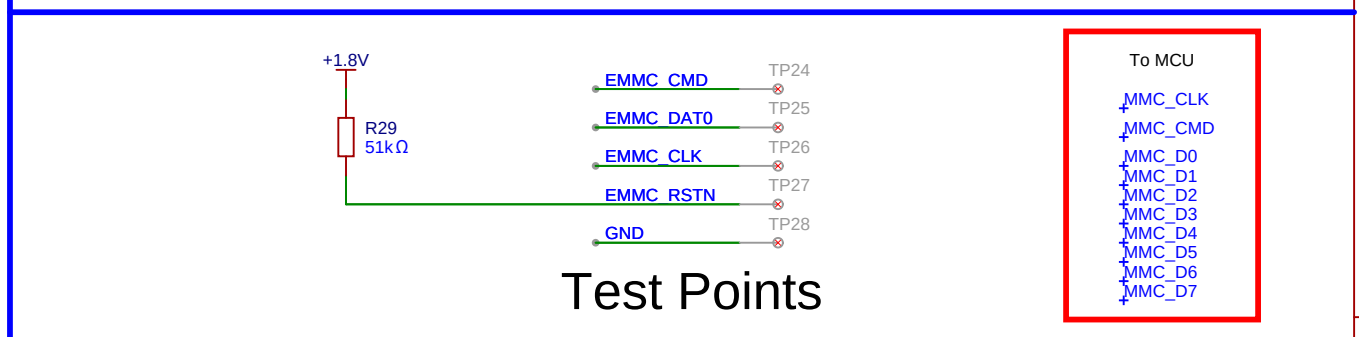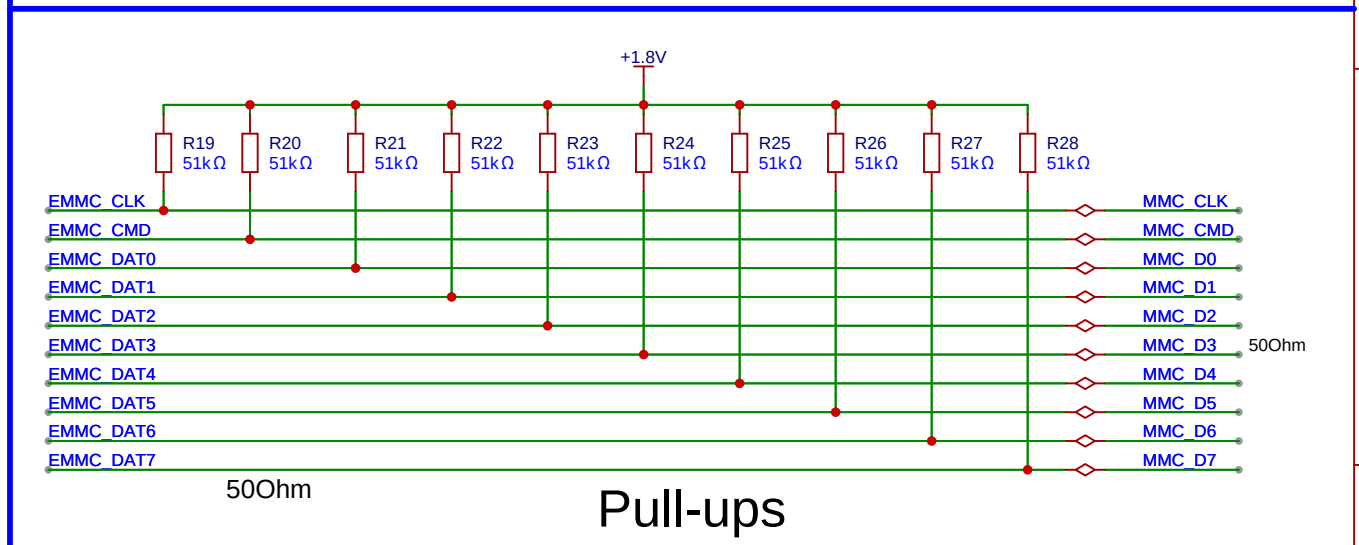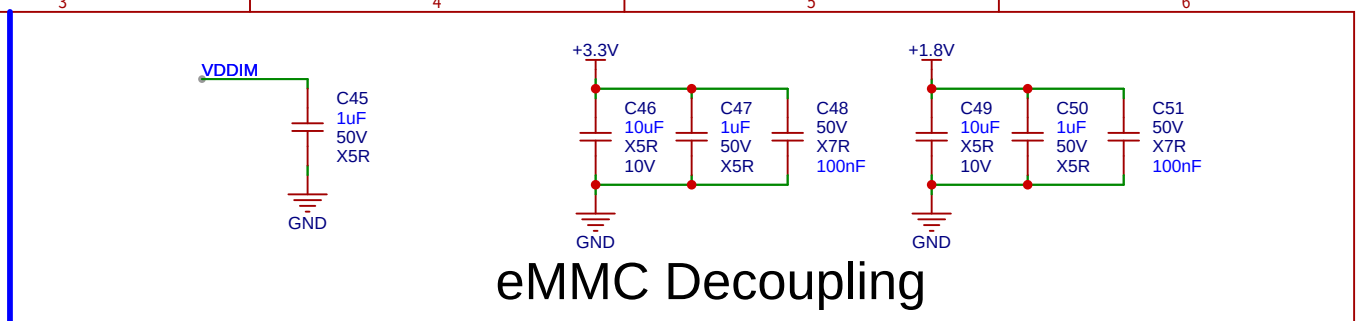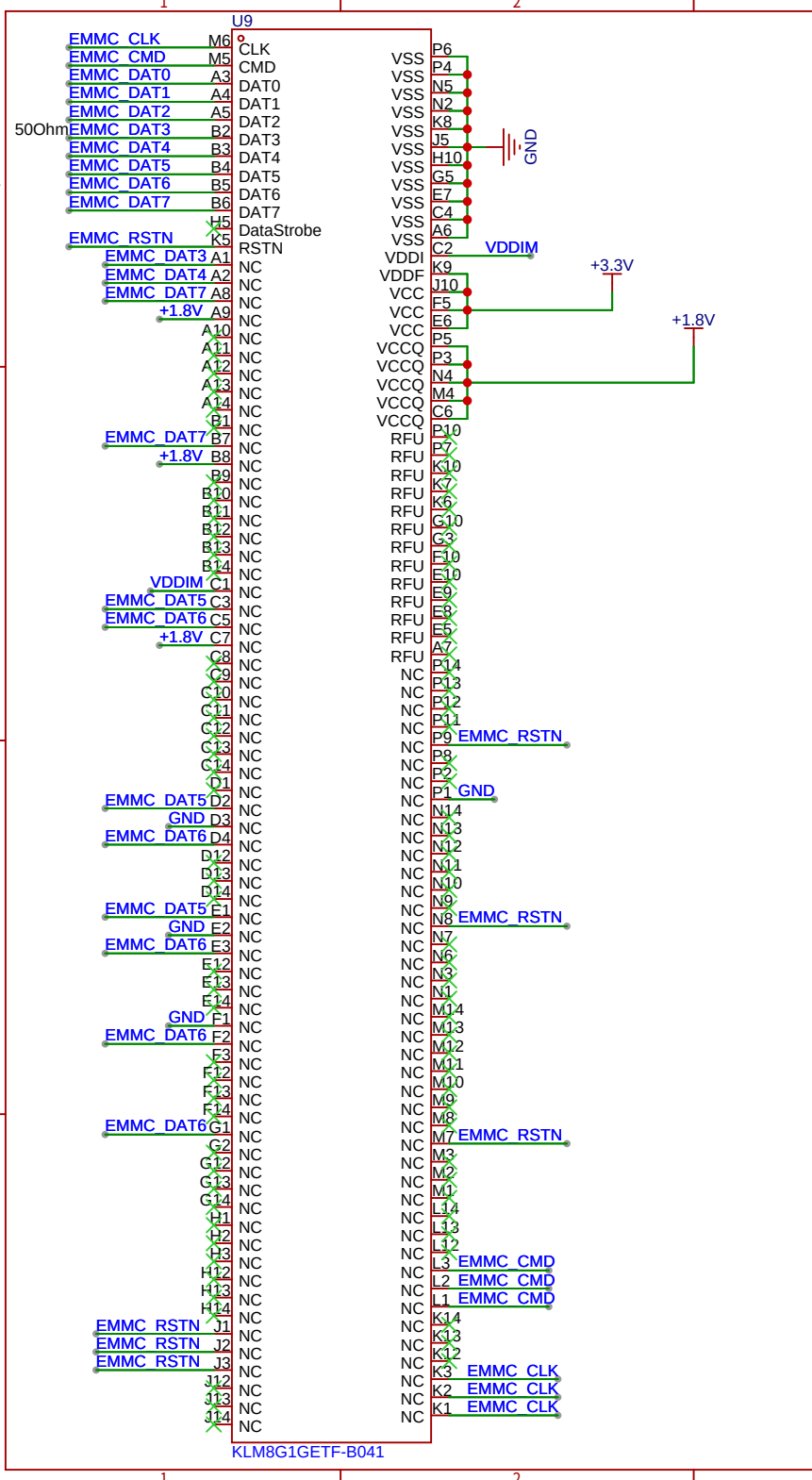


Schematic	Schematic		Create at	2026-01-15
Board	ESP32P4C6DevBoard		Update at	2026-02-01
Drawn	ESP32P4C6 Dev Board		Page	eMMC
Reviewed				
		Version	Size	Page 7 Total 9
		V1.0	A4	EasyEDA.com

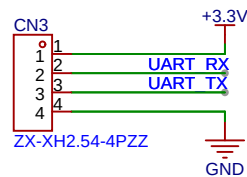

UART

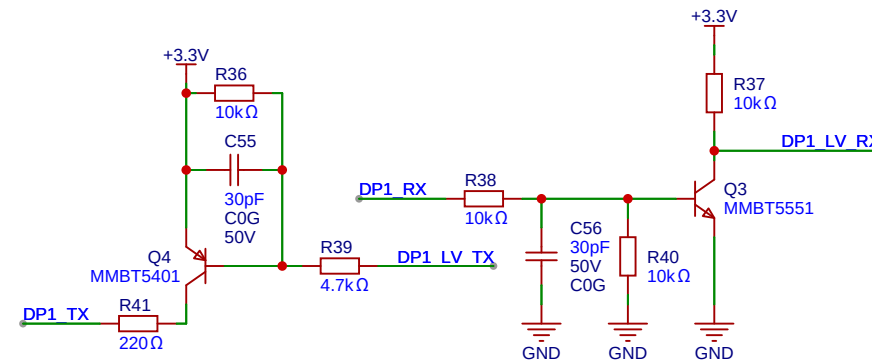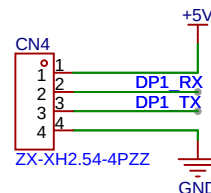

SERIAL TTL

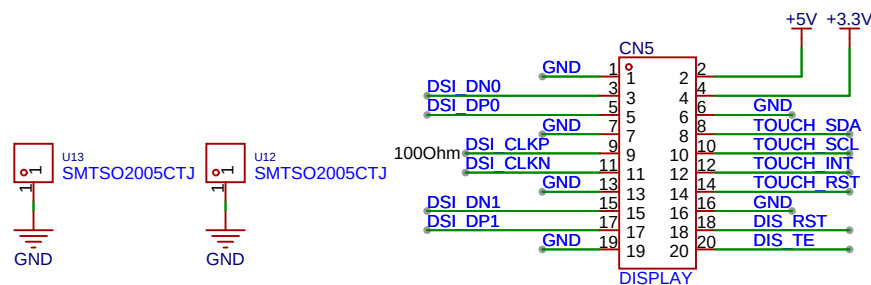


HRS DF40C-20DS-0.4V(51) <-> HRS DF40C-20DP-0.4V(51)

MIPI DSI

Display Connector

To MCU

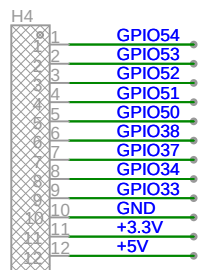DSI_DP0
DSI_DN0
DSI_DP1
DSI_DN1
DSI_CLKP
DSI_CLKN
UART_RX
UART_TX
DP1_LV_RX
DP1_LV_TX



Schematic	Schematic		Create at	2026-01-15
Board	ESP32P4C6DevBoard		Update at	2026-02-01
Drawn	ESP32P4C6 Dev Board			
Reviewed				
	Version	Size	Page 9 Total 9	
EasyEDA		V1.0	A4	EasyEDA.com